

KATHMANDU UNIVERSITY
End Semester Examination [C]
December, 2024

Level : B.E./B.Sc.
Year : II
Time : 2 hrs. 30mins.

Course : EEG 202
Semester : I
F. M. : 40

11 DEC 2024

SECTION "B"
[4 Q. × 10 = 40 marks]

Attempt ANY FOUR questions. Figure in the margin indicates the full mark. Students are required to answer in their own words as far as practicable. Calculators are not allowed.

1.
 - a. Differentiate between the standard form and the Canonical form of Boolean expression and minimize the following Boolean function using K-Map: [1+4]
 $F(A, B, C, D) = M_4 M_6 M_4 M_{11} M_{14} M_{15}$
 - b. Using 10's complement, perform the following subtraction: [2]
 $(470 - 231)_{10}$
 - c. Write truth table and design logic circuit for 3-bit binary to Gray code converter. [3]

2.
 - a. Design a combinational circuit using a ROM. The circuit accepts a three-bit number and outputs a binary number equal to the square of the input number. [5]
 - b. Design a logic circuit for 3 bit asynchronous up/down counter and explain the working mechanism with the help of timing diagram. [5]

3.
 - a. Derive the characteristic equation of T flip-flop and convert the T flip-flop into SR flip-flop with the help of excitation table. [2+3]
 - b. How does parity bit method help to detect the error? Design a logic circuit for even parity checker for 3-bit message and discuss the limitation of this method. [5]

4.
 - a. Design a logic circuit having four inputs W, X, Y, Z whose output is high whenever both Y and Z are high as long as W and X are either both low or both high. [5]
 - b. Write short notes on: [2.5x2]
 - i. Johnson counter
 - ii. Edge triggered flip-flop

5.
 - a. Explain the working of universal shift register with the help of circuit diagram. [4]
 - b. Design a sequential logic circuit specified by the state diagram of **figure1** using T flip-flop. [6]

P.T.O.

 


Figure1